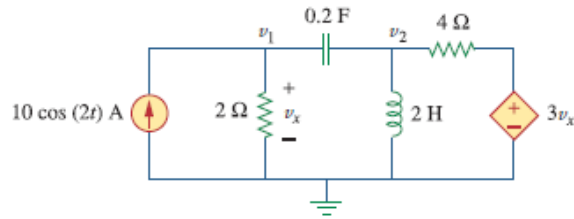


Question 1


Using Nodal analysis find v_1 and v_2 in the given circuit.



Ans: $v_1(t) = 11.325 \cos(2t + 60.01^\circ) V$ and $v_2(t) = 33.02 \cos(2t + 57.12^\circ) V$

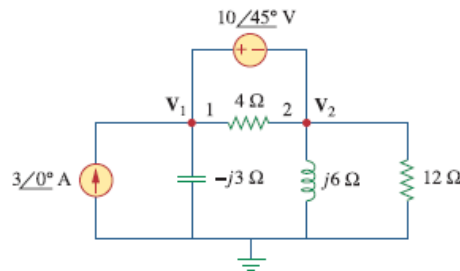Question 2


Compute v_1 and v_2 in the given circuit.



Ans: $v_1 = 25.78 \angle -70.48^\circ V$ and $v_2 = 31.41 \angle -87.18^\circ V$

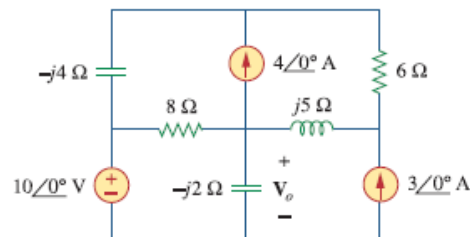Question 3


Solve for v_o in the circuit given below using mesh analysis.



Ans: $v_o = 9.756 \angle 222.32^\circ V$


Question 4

Find v_o in the circuit given below using superposition.

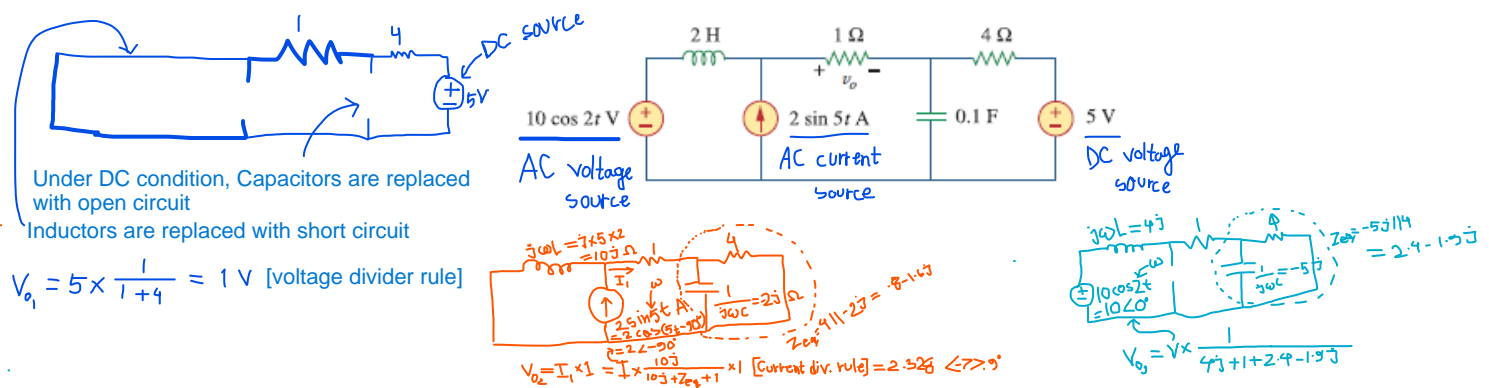

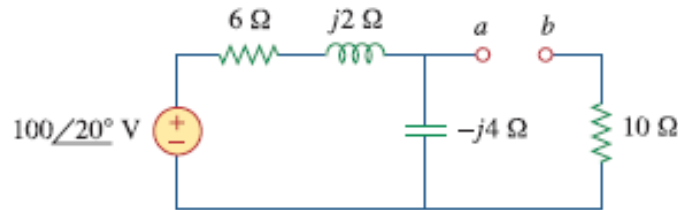Question 5

Obtain the Thevenin's equivalent at terminal a-b of the following circuit.




$$Z_{Th} = (6 + j2) \parallel (-j4) + 10$$

Ans: $Z_{Th} = 12.4 - j3.2 \Omega$, $V_{Th} = 63.24 \angle -51.57^\circ \text{ V}$.

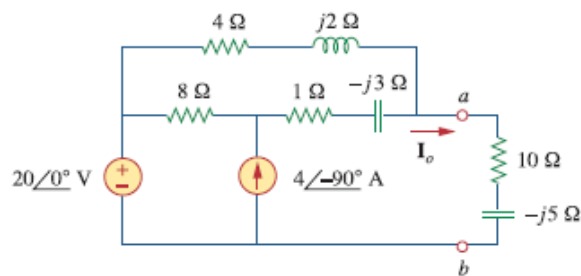Question 6

Determine the Norton's equivalent of the circuit in the given figure as seen from the terminal a and b. Use equivalent to find I_o .




Ans: $Z_N = 3.176 + j0.706 \Omega$, $I_N = 8.396 \angle -32.68^\circ \text{ A}$,
 $I_o = 1.9714 \angle -2.10^\circ \text{ A}$.

1.

$$10 \sin(2t) \longrightarrow 10 \angle 0^\circ, \quad \omega = 2$$

$$2 \text{ H} \longrightarrow j\omega L = j4$$
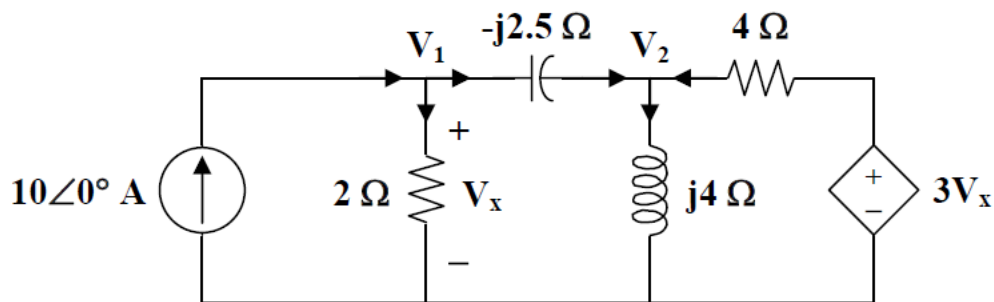
$$0.2 \text{ F} \longrightarrow \frac{1}{j\omega C} = -j2.5$$



At node 1, $10 = \frac{\mathbf{V}_1}{2} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j2.5}$

At node 2, $\frac{\mathbf{V}_2}{j4} = \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j2.5} + \frac{3\mathbf{V}_x - \mathbf{V}_2}{4}$ where $\mathbf{V}_x = \mathbf{V}_1$

Put (1) and (2) in matrix form.

$$\begin{bmatrix} 5 + j4 & -j4 \\ -(7.5 + j4) & 2.5 + j1.5 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \end{bmatrix}$$

where $\Delta = (5 + j4)(2.5 + j1.5) - (-j4)(-(7.5 + j4)) = 22.5 - j12.5 = 25.74 \angle -29.05^\circ$

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \frac{\begin{bmatrix} 2.5 + j1.5 & j4 \\ 7.5 + j4 & 5 + j4 \end{bmatrix}}{22.5 - j12.5} \begin{bmatrix} 100 \\ 0 \end{bmatrix}$$

$$\mathbf{V}_1 = \frac{2.5 + j1.5}{22.5 - j12.5}(100) = \frac{2.915 \angle 30.96^\circ}{25.74 \angle -29.05^\circ}(100) = 11.32 \angle 60.01^\circ$$

$$\mathbf{V}_2 = \frac{7.5 + j4}{22.5 - j12.5}(100) = \frac{8.5 \angle 28.07^\circ}{25.74 \angle -29.05^\circ}(100) = 33.02 \angle 57.12^\circ$$

2.

Nodes 1 and 2 form a supernode as shown in Fig. 10.5. Applying KCL at the supernode gives

$$3 = \frac{\mathbf{V}_1}{-j3} + \frac{\mathbf{V}_2}{j6} + \frac{\mathbf{V}_2}{12}$$

or

$$36 = j4\mathbf{V}_1 + (1 - j2)\mathbf{V}_2$$

But a voltage source is connected between nodes 1 and 2, so that

$$\mathbf{V}_1 = \mathbf{V}_2 + 10 \angle 45^\circ$$

Substituting Eq. (10.2.2) in Eq. (10.2.1) results in

$$36 - 40 \angle 135^\circ = (1 + j2)\mathbf{V}_2 \Rightarrow \mathbf{V}_2 = 31.41 \angle -87.18^\circ \text{ V}$$

From Eq. (10.2.2),

$$\mathbf{V}_1 = \mathbf{V}_2 + 10 \angle 45^\circ = 25.78 \angle -70.48^\circ \text{ V}$$

3.

As shown in Fig. 10.10, meshes 3 and 4 form a supermesh due to the current source between the meshes. For mesh 1, KVL gives

$$-10 + (8 - j2)\mathbf{I}_1 - (-j2)\mathbf{I}_2 - 8\mathbf{I}_3 = 0$$

or

$$(8 - j2)\mathbf{I}_1 + j2\mathbf{I}_2 - 8\mathbf{I}_3 = 10$$

For mesh 2,

$$\mathbf{I}_2 = -3$$

For the supermesh,

$$(8 - j4)\mathbf{I}_3 - 8\mathbf{I}_1 + (6 + j5)\mathbf{I}_4 - j5\mathbf{I}_2 = 0$$

Due to the current source between meshes 3 and 4, at node A,

$$\mathbf{I}_4 = \mathbf{I}_3 + 4$$


Instead of solving the above four equations, we reduce them to two by elimination.

combining above equations

$$(8 - j2)\mathbf{I}_1 - 8\mathbf{I}_3 = 10 + j6$$

Combining Eqs. (10.4.2) to (10.4.4),
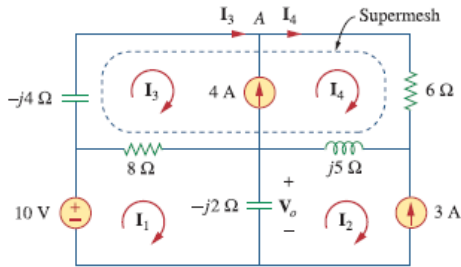
$$-8\mathbf{I}_1 + (14 + j)\mathbf{I}_3 = -24 - j35$$



$$\begin{bmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10 + j6 \\ -24 - j35 \end{bmatrix}$$

We obtain the following determinants

$$\Delta = \begin{vmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{vmatrix} = 112 + j8 - j28 + 2 - 64 = 50 - j20$$

$$\begin{aligned} \Delta_1 &= \begin{vmatrix} 10 + j6 & -8 \\ -24 - j35 & 14 + j \end{vmatrix} = 140 + j10 + j84 - 6 - 192 - j280 \\ &= -58 - j186 \end{aligned}$$

Current \mathbf{I}_1 is obtained as

$$\mathbf{I}_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j186}{50 - j20} = 3.618 \angle 274.5^\circ \text{ A}$$

The required voltage \mathbf{V}_0 is




$$\begin{aligned} \mathbf{V}_0 &= -j2(\mathbf{I}_1 - \mathbf{I}_2) = -j2(3.618 \angle 274.5^\circ + 3) \\ &= -7.2134 - j6.568 = 9.756 \angle 222.32^\circ \text{ V} \end{aligned}$$

4.

$$10 \cos 2t \Rightarrow 10 \angle 0^\circ, \quad \omega = 2 \text{ rad/s}$$

$$2 \text{ H} \Rightarrow j\omega L = j4 \, \Omega$$
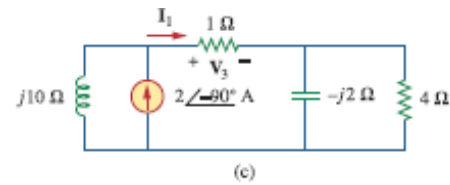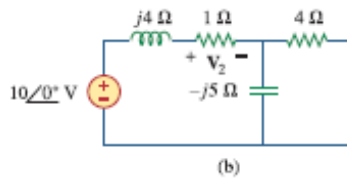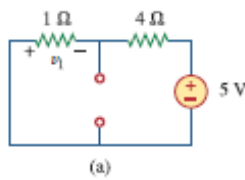
$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega C} = -j5 \, \Omega$$



$$-v_1 = \frac{1}{1 + 4}(5) = 1 \text{ V}$$

$$\mathbf{V}_2 = \frac{1}{1 + j4 + \mathbf{Z}}(10 \angle 0^\circ) = \frac{10}{3.439 + j2.049} = 2.498 \angle -30.79^\circ$$

$$2 \sin 5t \Rightarrow 2 \angle -90^\circ, \quad \omega = 5 \text{ rad/s}$$

$$2 \text{ H} \Rightarrow j\omega L = j10 \, \Omega$$

$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega C} = -j2 \, \Omega$$

$$\mathbf{Z}_1 = -j2 \parallel 4 = \frac{-j2 \times 4}{4 - j2} = 0.8 - j1.6 \, \Omega$$


By current division,

$$\mathbf{I}_1 = \frac{j10}{j10 + 1 + \mathbf{Z}_1}(2 \angle -90^\circ) \text{ A}$$

$$\mathbf{V}_3 = \mathbf{I}_1 \times 1 = \frac{j10}{1.8 + j8.4}(-j2) = 2.328 \angle -80^\circ \text{ V}$$

$$v_o(t) = -1 + 2.498 \cos(2t - 30.79^\circ) + 2.33 \sin(5t + 10^\circ) \text{ V}$$

5.

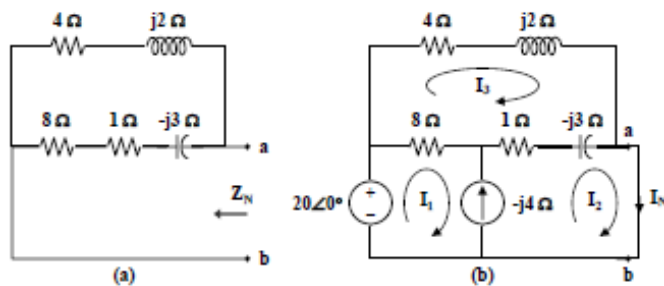

$$Z_N = (4 + j2) \parallel (9 - j3) = \frac{(4 + j2)(9 - j3)}{13 - j}$$

$$Z_N = \underline{\underline{3.176 + j0.706\ \Omega}}$$

To find I_N , short-circuit terminals a-b as shown in Fig. (b). Notice that meshes 1 and 2 form a supermesh.

$$\text{For the supermesh, } -20 + 8I_1 + (1 - j3)I_2 - (9 - j3)I_3 = 0 \quad (1)$$

$$\text{Also, } I_1 = I_2 + j4 \quad (2)$$


$$\text{For mesh 3, } (13 - j)I_3 - 8I_1 - (1 - j3)I_2 = 0 \quad (3)$$

Solving for I_2 , we obtain

$$I_N = I_2 = \frac{50 - j62}{9 - j3} = \frac{79.65\angle -51.11^\circ}{9.487\angle -18.43^\circ}$$

$$I_N = \underline{\underline{8.396\angle -32.68^\circ\ \text{A}}}$$

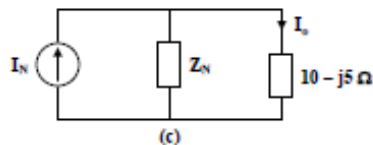Using the Norton equivalent, we can find I_o as in Fig. (c).



By current division,

$$I_o = \frac{Z_N}{Z_N + 10 - j5} I_N = \frac{3.176 + j0.706}{13.176 - j4.294} (8.396\angle -32.68^\circ)$$

$$I_o = \frac{(3.254\angle 12.53^\circ)(8.396\angle -32.68^\circ)}{13.858\angle -18.05^\circ}$$

$$I_o = \underline{\underline{1.971\angle -2.10^\circ\ \text{A}}}$$