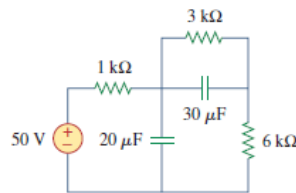


### Question 1


Under dc conditions, find the energy stored in the capacitors in given Fig.



Ans: 20.25 mJ, 3.375 mJ.
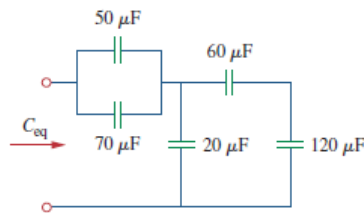
### Question 2


Find the equivalent capacitance seen at the terminals of the circuit in given Fig.



Ans: 40 μF.
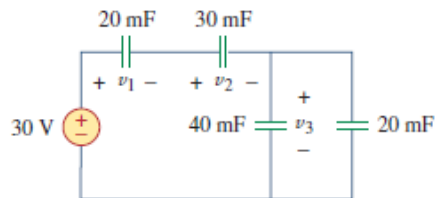
### Question 3

For the circuit in Fig. given, find the voltage across each capacitor.



Ans: 10V, 5V, and 5V.


### Question 4

The terminal voltage of a 2-H inductor is  $v = 10(1 - t)V$ . Find the current flowing through it at  $t=4s$  and the energy stored in it at  $t=4s$ . Assume  $i(0) = 2A$

Ans: -18A, and 320J.
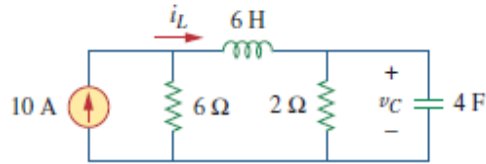
### Question 5


Determine  $v_c$  and  $i_L$  the energy stored in the capacitor and inductor in the circuit of given figure under dc conditions.



Ans: 15 V, 7.5 A, 450 J, 168.75 J.
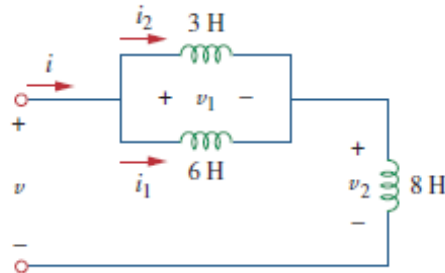
### Question 6

In the circuit of given figure  $i_1(t) = 0.6e^{-2t}$  A. If  $i(0) = 1.4$  A, find: (a)  $i_2(0)$ , (b)  $i_2(t)$  and  $i(t)$  (c)  $v_1(t)$ ,  $v_2(t)$ , and  $v(t)$ .



Ans: (a) 0.8 A, (b)  $(-0.4 + 1.2e^{-2t})$  A,  $(-0.4 + 1.8e^{-2t})$  A, (c)  $-36e^{-2t}$  V,  $-7.2e^{-2t}$  V,  $-28.8e^{-2t}$  V.

### Question 8

A 4-mF capacitor has the current waveform shown in the given Fig. Assuming that  $v_o(0) = 10$  V, sketch the voltage waveform  $v(t)$ .

