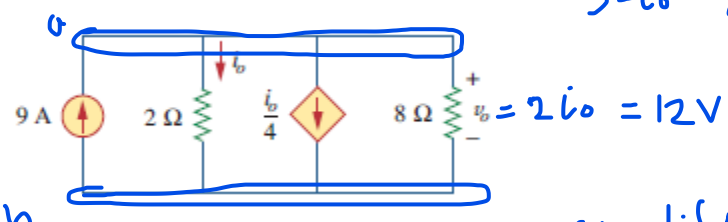



Step 1: Simplify the circuit  
a. Marrow down the nodes.
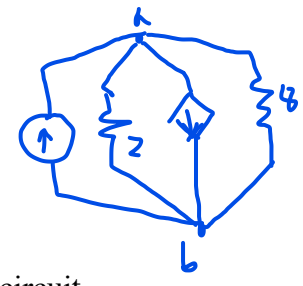
### Question 1

Find  $v_o$  and  $i_o$  in the circuit given below:




$$9 - i_o - \frac{i_o}{4} - \frac{2i_o}{8} = 0 \quad \therefore i_o = 6A$$


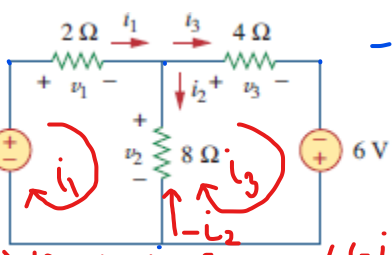
### Question 2

Find the currents and voltages in the circuit shown in the following circuit

• Loop direction is taken opposite to  $i_2$ 's direction. ( $-i_2$ )





$$\begin{aligned} -10 + 2i_1 + 8i_2 &= 0 \\ 4i_3 - 6 - 8(-i_2) &= 0 \\ i_1 - i_3 - i_2 &= 0 \end{aligned} \quad \left| \begin{aligned} i_1 &= 3A \\ i_2 &= 0.5A \\ i_3 &= 2.5A \end{aligned} \right.$$

$$V_1 = 6V, V_2 = 4V, V_3 = 10V$$
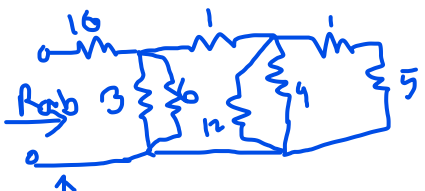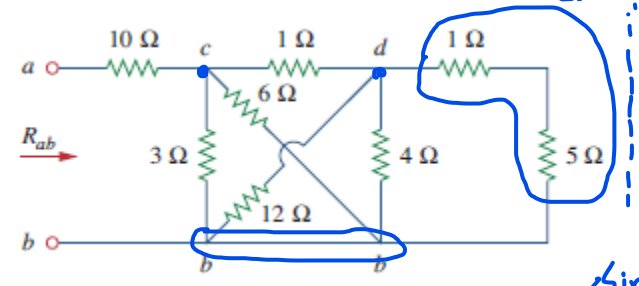
### Question 3


Find  $R_{ab}$  for the circuit shown below:



$$R_{ab} = 11.2 \Omega$$
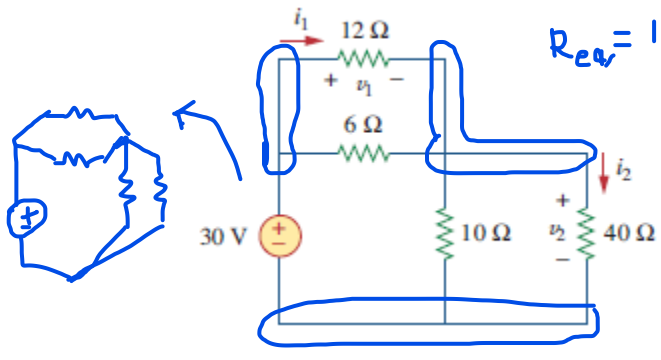
### Question 4

Find  $v_1$  and  $v_2$  in the circuit shown in following figure. Also calculate  $i_1$  and  $i_2$  and the power dissipated in the 12Ω and 40Ω resistors.




$$R_{eq} = 12 \Omega \quad \therefore I = \frac{30}{12} = 2.5A$$

$$\therefore i_1 = 2.5 \times \frac{6}{12+6} = 0.833A \quad ; \quad v_1 = 10V$$

$$i_2 = 2.5 \times \frac{10}{10+40} = 0.5A \quad ; \quad v_2 = 20V$$
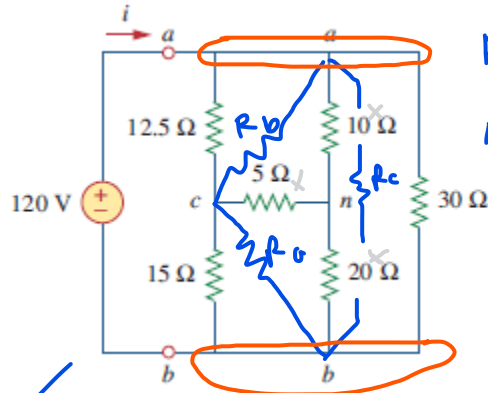
### Question 5

Obtain the equivalent resistance  $R_{ab}$  for the circuit in following figure and use it to find current  $i$ .



$$R_a = \frac{10 \times 20 + 10 \times 5 + 5 \times 20}{10} = 35 \Omega$$

$$R_b = \frac{350}{20} = 17.5 \Omega$$


$$R_c = \frac{350}{5} = 70 \Omega$$

$$R_{ab} = 0.63 \Omega$$

$$i = \frac{120}{9.63} = 12.45 A$$
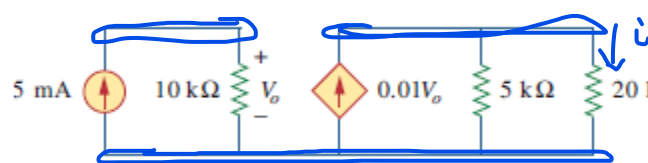
### Question 6

For the network in the given figure, find the current, voltage, and power associated with the 20-kΩ resistor.




$$V_o = 10000 \times 5 \times 10^{-3} = 50 V$$

$$I_o = 0.01 V_o = 0.5 A$$

$$i = I_o \times \frac{5000}{5000 + 20000} = 0.1 A$$

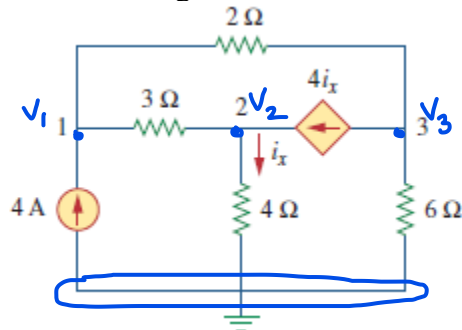
### Question 7

Find the voltages at the three non-reference nodes in the circuit below.


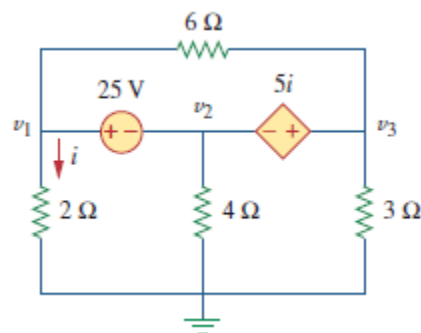
### Question 8

Find  $v_1$ ,  $v_2$  and  $v_3$  in the circuit of following figure using nodal analysis.



### Question 9

For the circuit in the given circuit, find  $i_1$  to  $i_4$  using mesh analysis.

