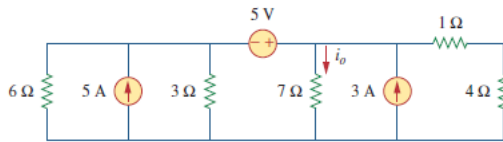


### Question 1


Find  $i_0$  in the circuit shown below, use source transformation:



Ans: 1.78 A.
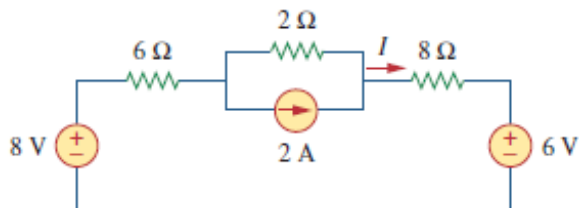
### Question 2


Find  $I$  in the circuit of the following Fig. using the superposition principle.



Ans: 375 mA
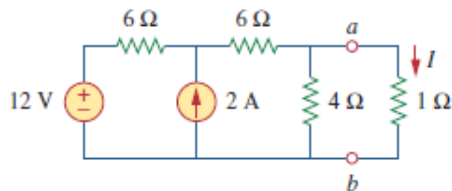
### Question 3


Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit of given Fig. Then find  $I$ .



Ans: 6 V, 3Ω, and 1.5 A.
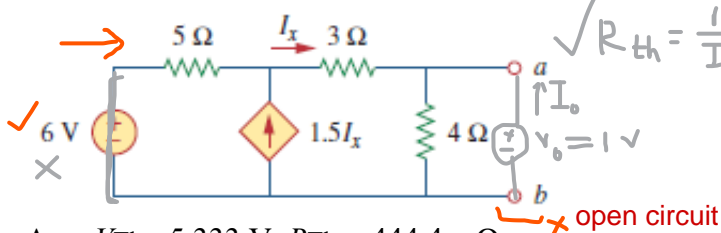
### Question 4

Find the Thevenin equivalent circuit of the circuit in given Fig. to the left of the terminals.



Ans:  $V_{Th} = 5.333$  V,  $R_{Th} = 444.4$  mΩ.

$$-6 + 5(I_x - 1.5I_x) + 3I_x + 4I_x = 0$$

$$\therefore I_x = 1.33 \text{ A}$$

$$\therefore V_{Th} = 4I_x = 5.33 \text{ V}$$

$$R_{Th} = \frac{1}{I_0} = 0.4444 \Omega$$

$$5(I_x - 1.5I_x) + 3I_x + 1 = 0$$

$$\therefore I_x = -2 \text{ A}$$

★ voltage across 4 ohm is 1 V

$$\therefore I_{4\Omega} = \frac{1}{4} \text{ A}$$


$$\therefore I_0 = I_{4\Omega} - I_x = 2.25$$

$$I = 4.875$$

$$I_x = 10$$
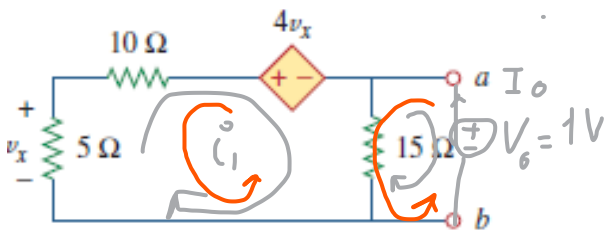
### Question 5

Obtain the Thevenin equivalent of the circuit in following Fig.



$$R_{th} = \frac{V_o}{I_o} = \frac{1}{I_o}$$

$$5i_1 + 10i_1 + 4(-5i_1) + 15(i_1 + I_o) = 0$$

$$1 + 15(-I_o - i_1) = 0$$

Ans:  $V_{Th} = 0$  V,  $R_{Th} = -7.5 \Omega$ .


$$15(i_1 - I_o) - 4(5i_1) + 10i_1 + 5i_1 = 0 \Rightarrow I_o = -\frac{2}{15} \text{ A}$$

$$15(I_o - i_1) - 1 = 0 \Rightarrow I_o = -\frac{2}{15}$$

$$\therefore R_{th} = -7.5 \Omega$$
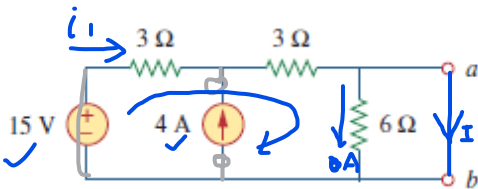
### Question 6

Find the Norton equivalent circuit for the circuit in the given Fig., at terminals a-b.



$$R_N = (3+3) \parallel 6 = 3 \Omega$$

$$I_N = 4.5 \text{ A}$$

Ans:  $R_N = 3 \Omega$ ,  $I_N = 4.5 \text{ A}$ .

$$-15 + 3i_1 + 3(i_1 + 4) + 6(0) = 0$$


$$\therefore i_1 = 0.5 \text{ A}$$

$$\therefore I_N = i_1 + 4 = 4.5$$

### Question 7

Find the Norton equivalent circuit of the circuit in the following Fig. at terminals a-b.


source transformation

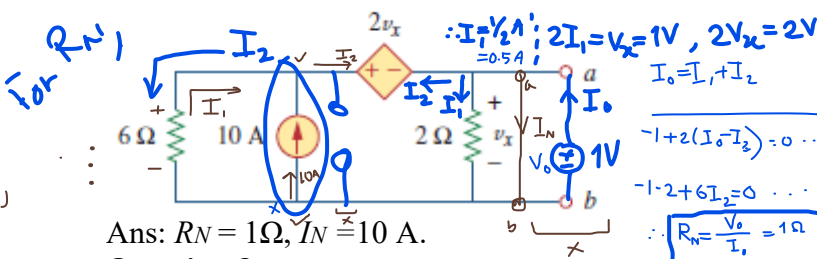

Ans:  $R_N = 1 \Omega$ ,  $I_N = 10 \text{ A}$ .
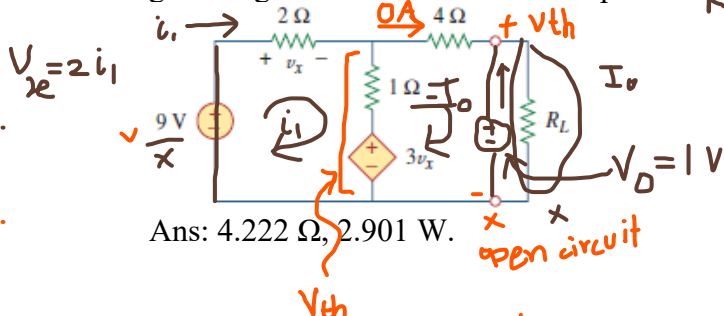
### Question 8

Determine the value of  $R_L$  that will draw the maximum power from the rest of the circuit in the given Fig. Calculate the maximum power.



Ans:  $4.222 \Omega$ ,  $2.901 \text{ W}$ .

$$R_L = R_{th} = \frac{1}{I_o} = 4.22 \Omega$$

$$2i_1 + 1(i_1 - (-I_o)) + 3(2i_1) = 0$$

$$-3(2i_1) + 1(-I_o - i_1) + 4(-I_o) + 1 = 0$$

$$\therefore I_o = \frac{9}{38} \text{ A}$$

$$P_{L, \max} = \frac{V_{th}^2}{4R_{th}} = 2.75 \text{ W}$$

$$-9 + 2i_1 + 1i_1 + 3(2i_1) = 0 \Rightarrow i_1 = 1 \text{ A}$$

$$\therefore V_{th} = 1 \times 1 + 3 \times 2 \times 1 = 7 \text{ V}$$